

Easy way to turn on or off a single circuit (light).

Cut section of red (+) out to break the circuit

Lay switch over cutout and “Bam Bam grommets into two tabs

**Same as above but I soldered to tabs to the red run
Once attached, the switch will open or close (make or break) the red side of circuit.**